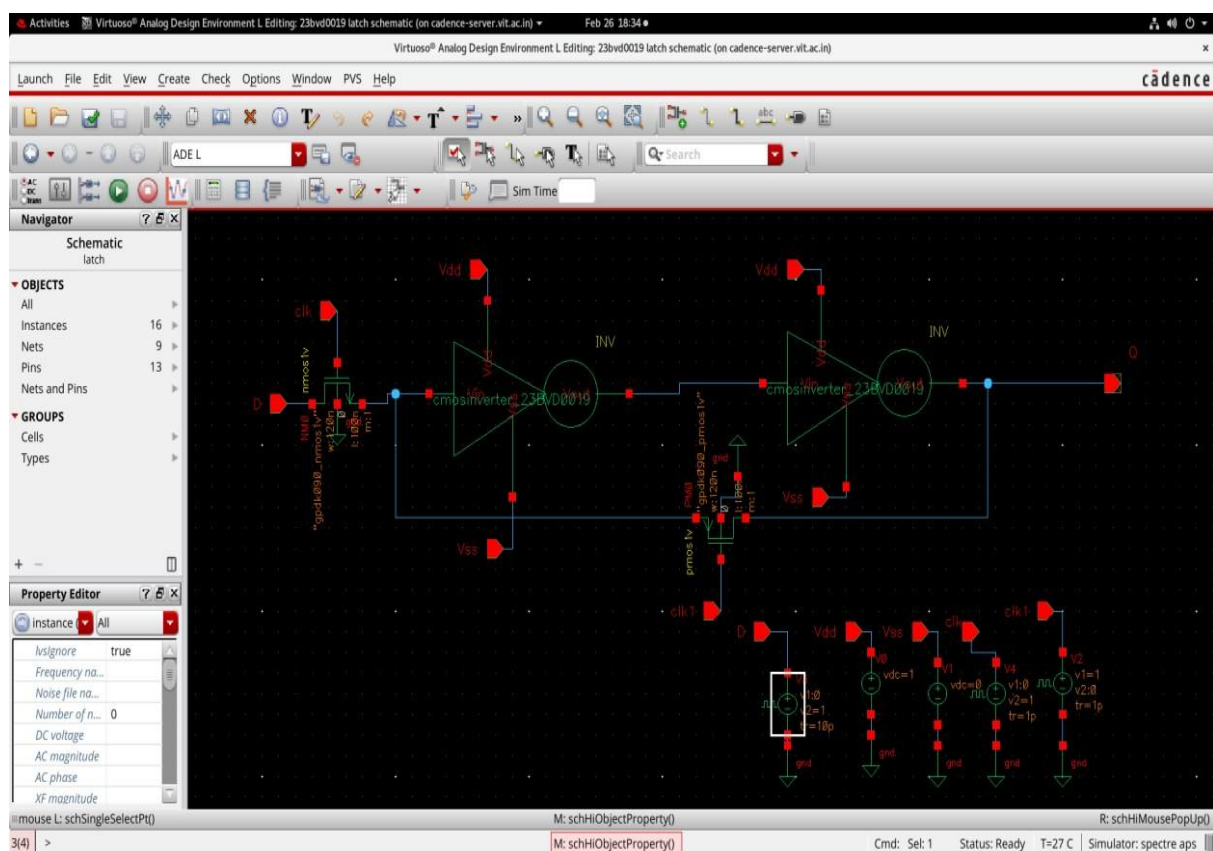


# IMPLEMENTATION OF D-LATCH, D-FLIP FLOP, SISO REGISTER, AND D TO T FLIP FLOP USING CADENCE VIRTUOSO

## D-LATCH


Circuit Diagram:




Output Waveform:



# D-FLIP FLOP:


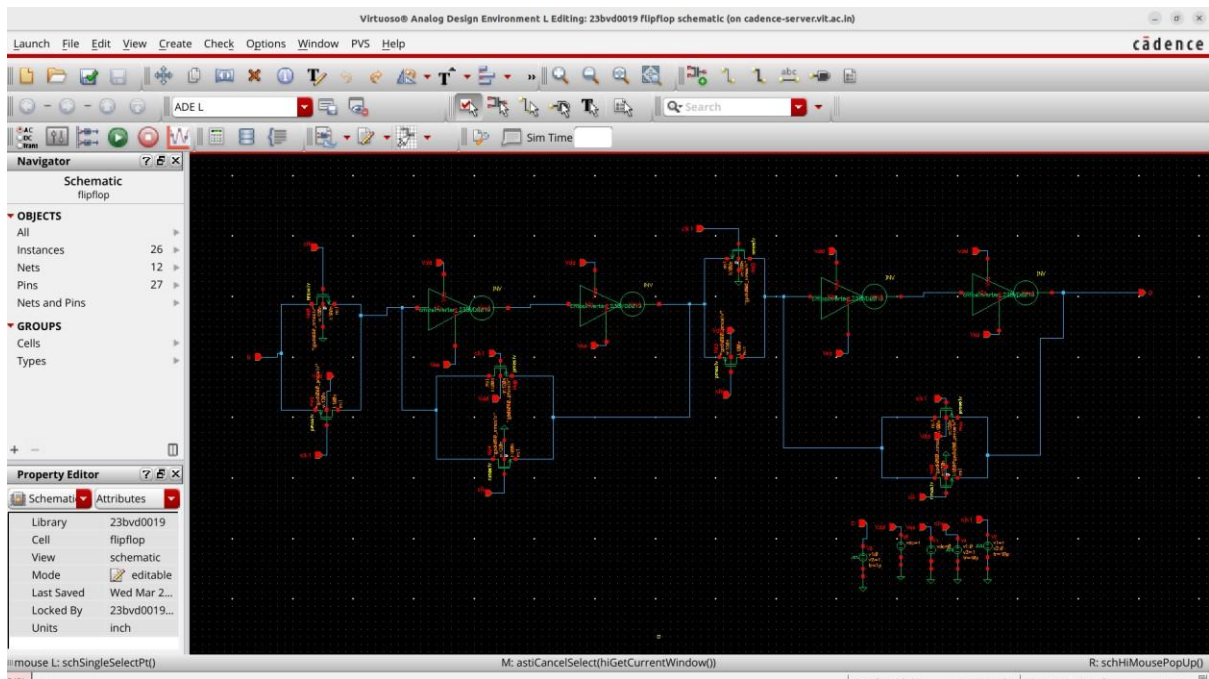


## Output Waveform:

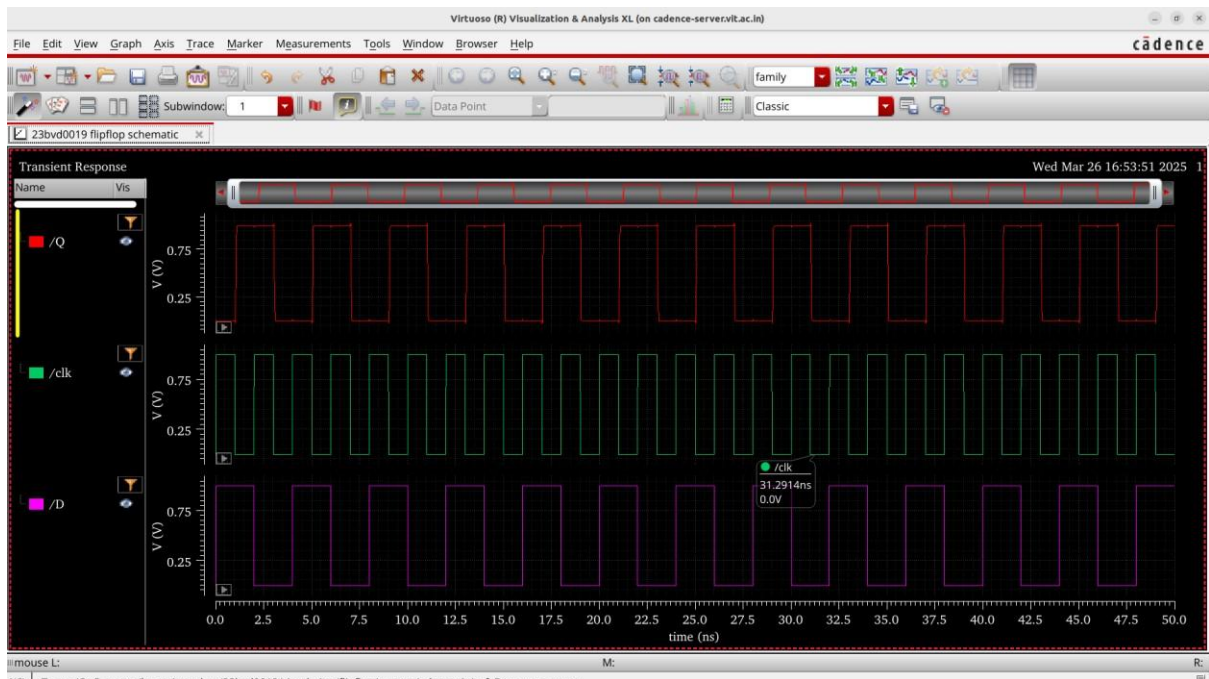


# SERIES IN SERIES OUT:

## Schematic:

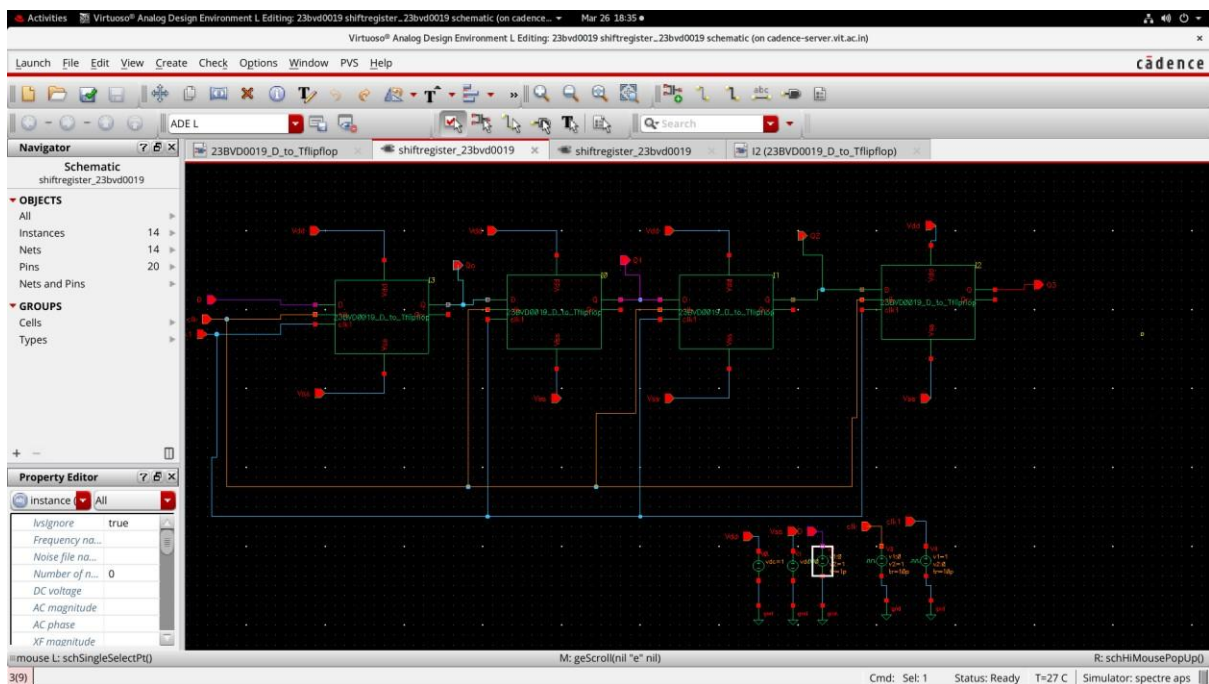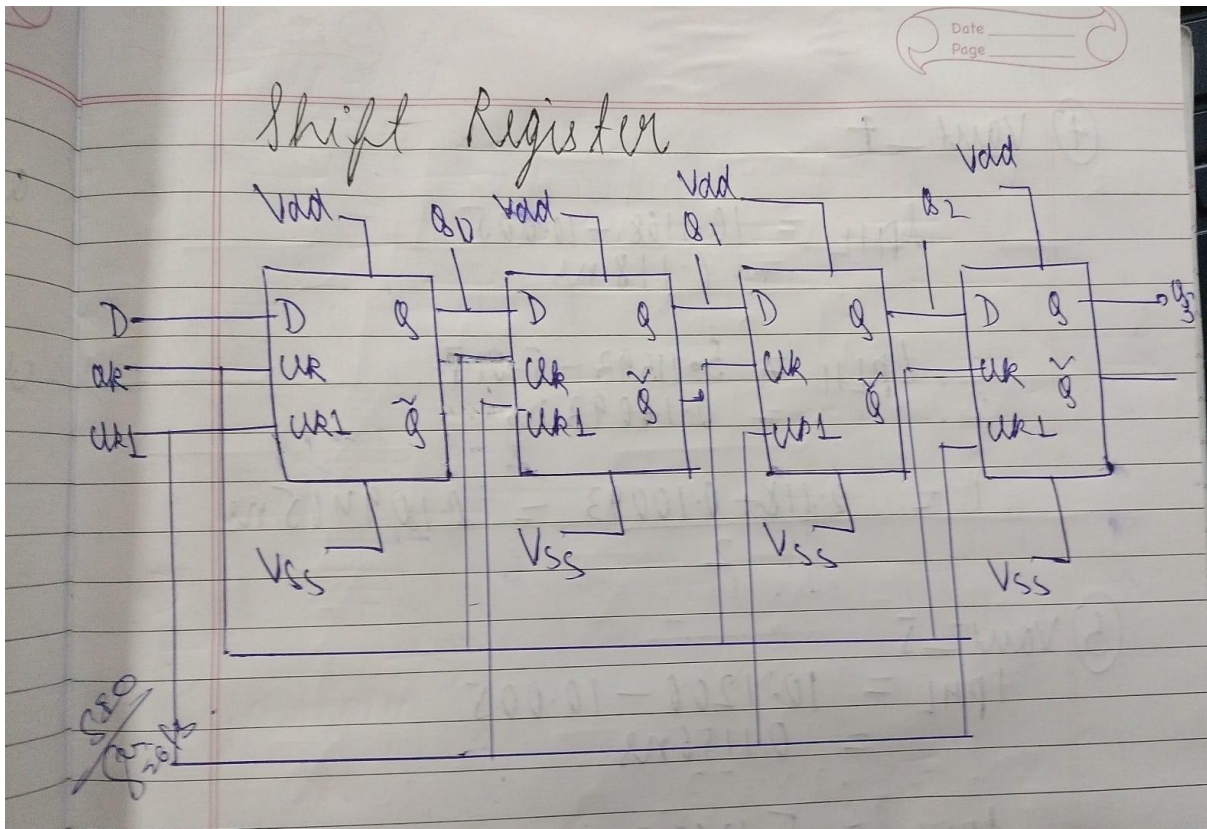




## Output Waveform :

 

# D TO T – FLIP FLOP Schematic:

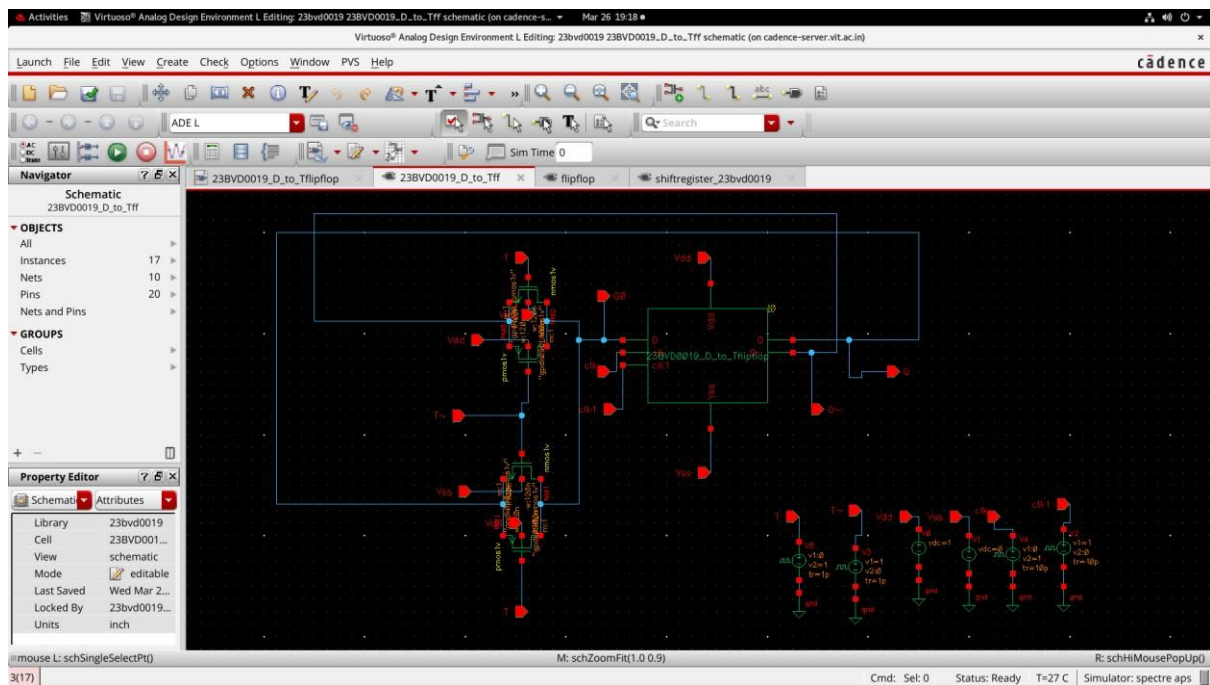

# Waveform Generation:

